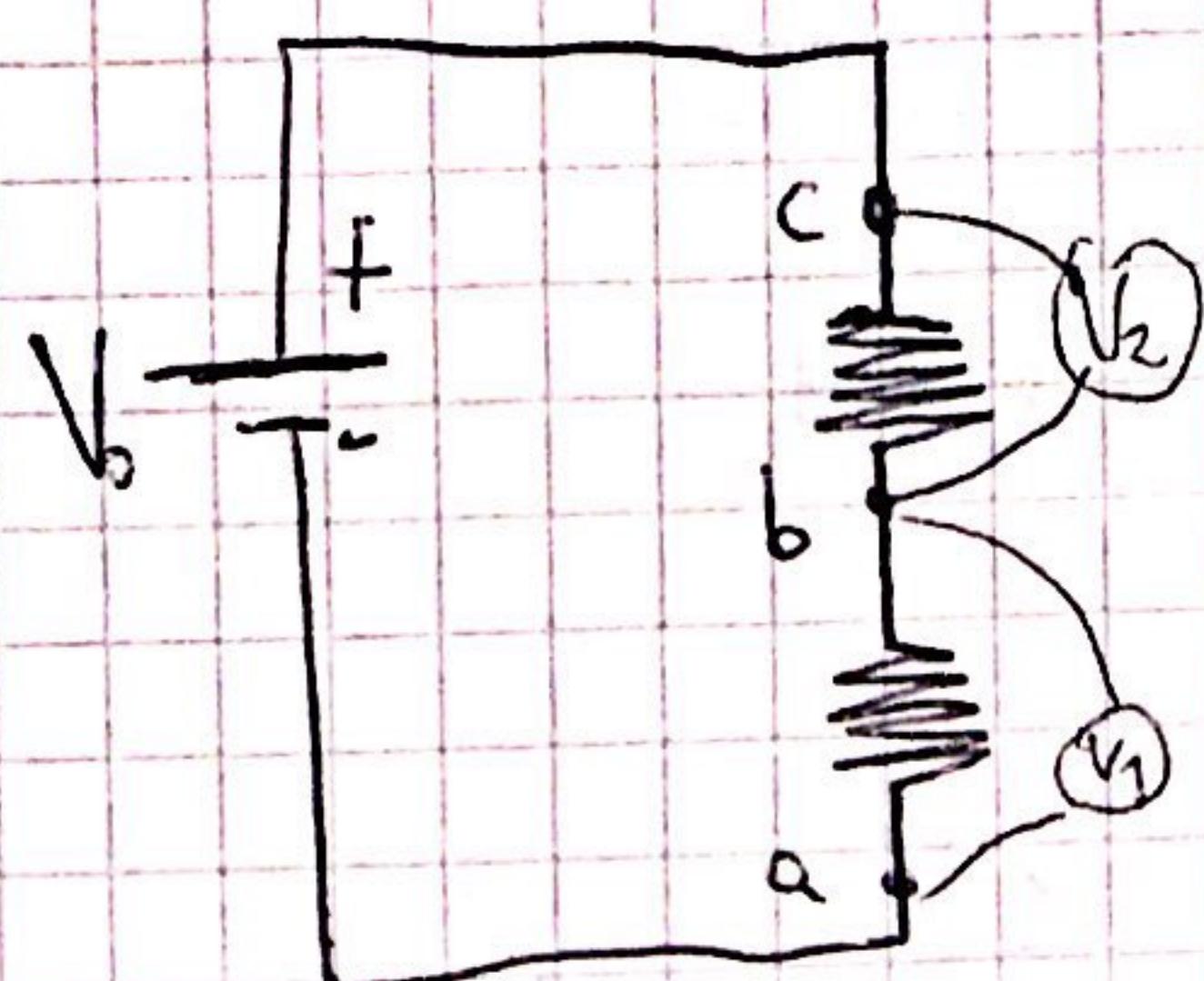


PRACTICO 7

1

a)



) Voltímetros:

$$V_o = V_1 + V_2 = \underbrace{C \cdot R_1}_{\text{Cargas}} + \underbrace{i \cdot R_2}_{\text{septencial}} \Rightarrow i = \frac{V_o}{R_1 + R_2}$$

Cargas
septencial


$$\cdot V_1 = \frac{V_o \cdot R_1}{R_1 + R_2}$$

$$\cdot V_2 = \frac{V_o \cdot R_2}{R_1 + R_2}$$

b) Dado que están en serie:

$$R_{eq} = R_1 + R_2$$

2

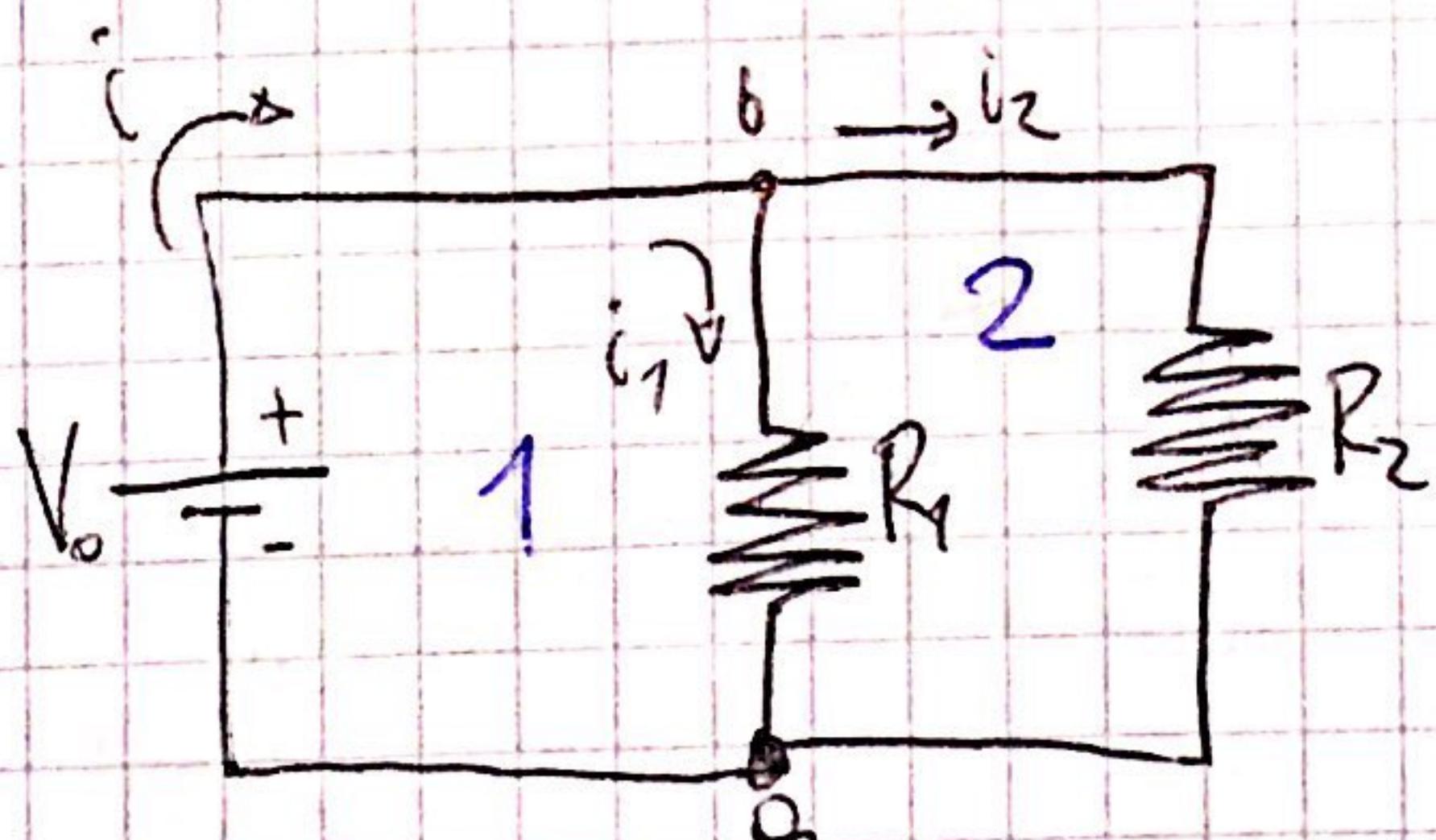

a)

Leyes de Kirchoff:

$$\text{Por malla 1: } V_o = V_1$$

$$\text{Por malla 2: } 0 = V_2 - V_1 \Rightarrow V_2 > V_1 = V_o$$

b)

$$\text{Por malla 1: } V_o = i_1 \cdot R_1 \Rightarrow i_1 = \frac{V_o}{R_1}$$

$$\begin{aligned} \text{Por malla 2: } 0 &= i_2 R_2 - i_1 R_1 \\ &= i_2 R_2 - V_o \Rightarrow i_2 = \frac{V_o}{R_2} \end{aligned}$$

$$\text{Además: } i = i_1 + i_2 = V_o \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

c)

$$P_1 = i_1^2 R_1 = \left(\frac{V_o}{R_1} \right)^2 \cdot R_1 = \frac{V_o^2}{R_1}$$


$$P_2 = i_2^2 R_2 = \left(\frac{V_o}{R_2} \right)^2 \cdot R_2 = \frac{V_o^2}{R_2}$$

d)


$$R_{eq} = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1}, \quad \text{Pues están en paralelo}$$

3

a)

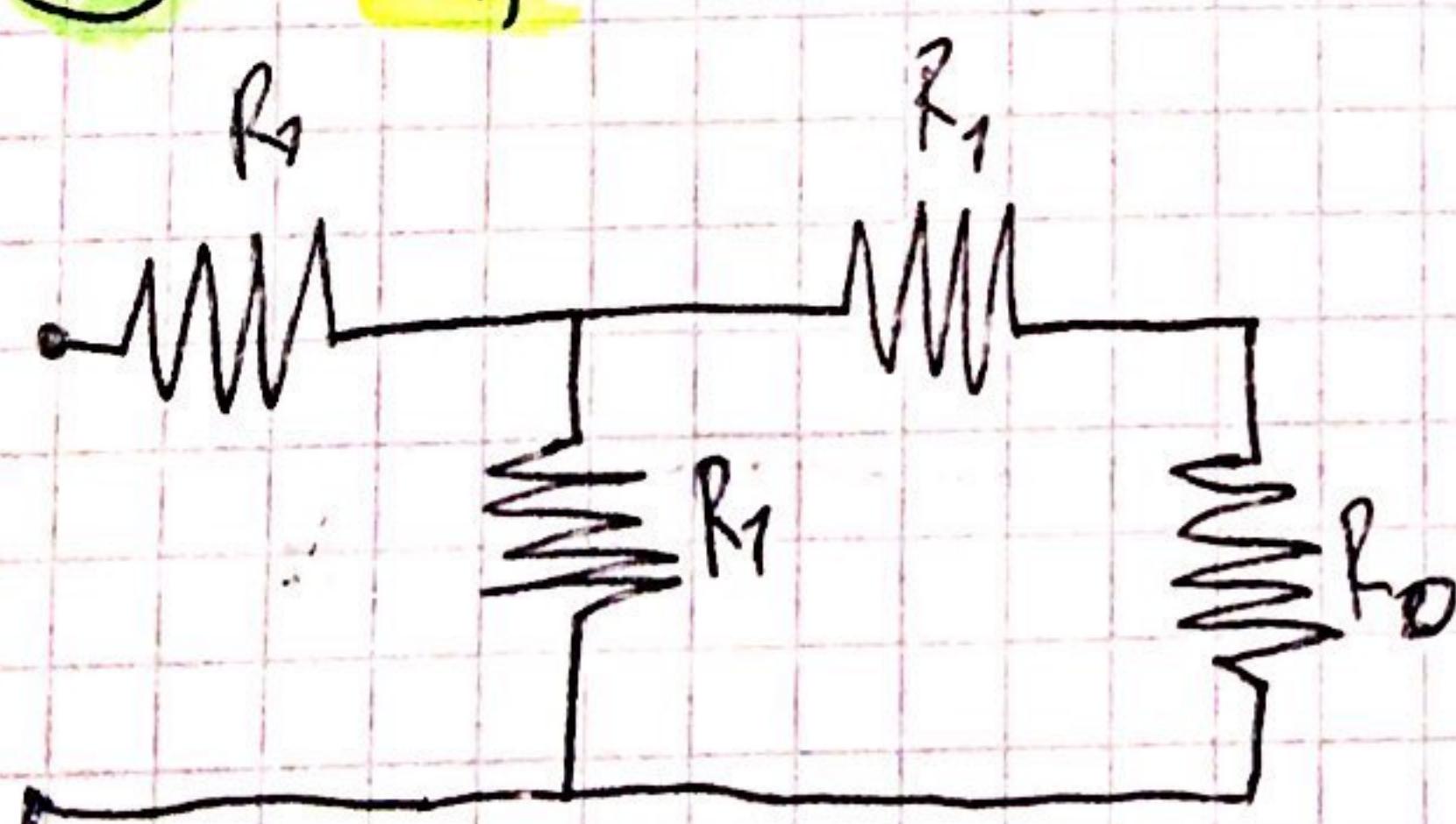


$$R'_{eq} = R_1 + R_L$$

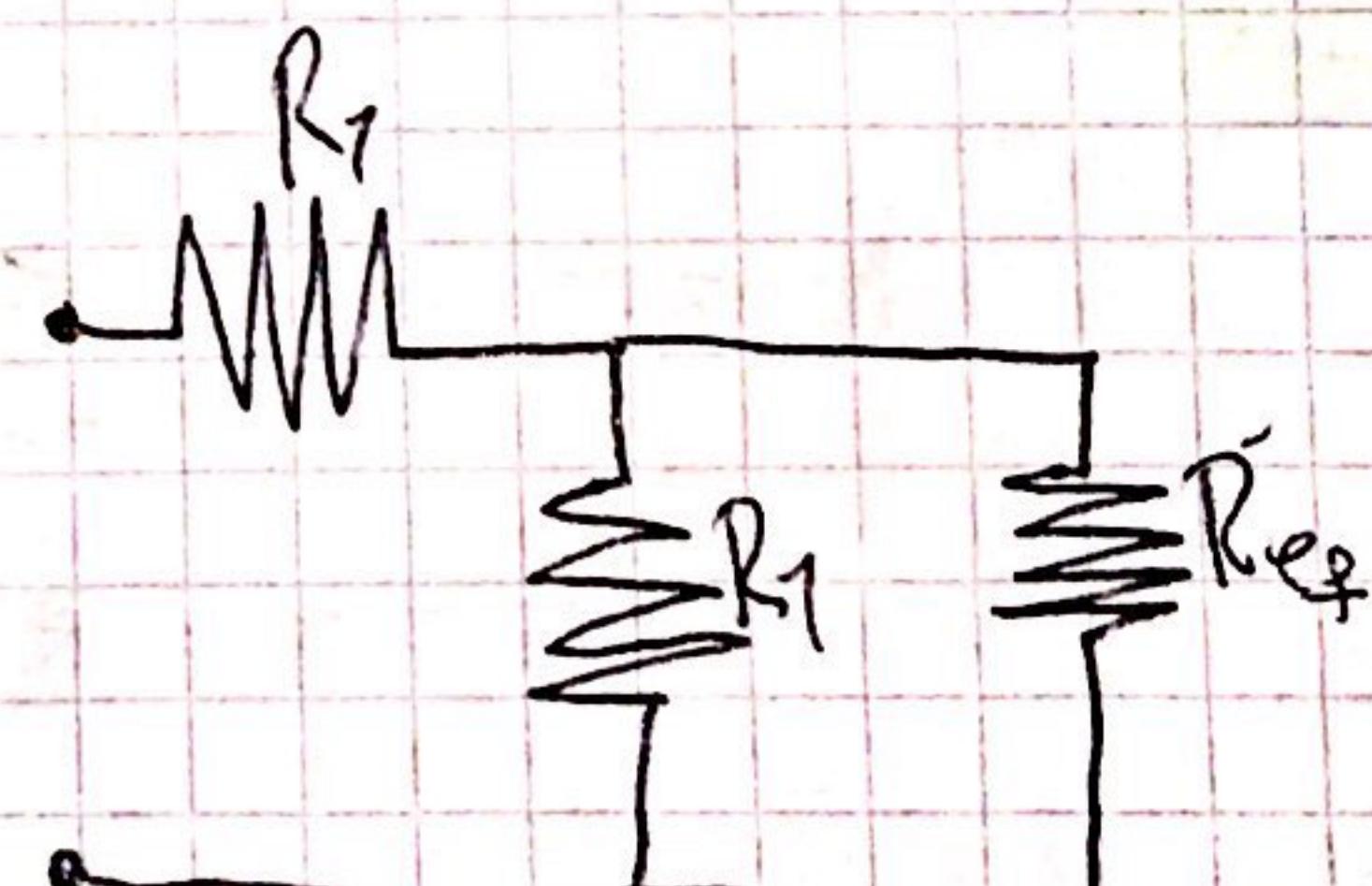

$$R''_{eq} = \left(\frac{1}{R_1} + \frac{1}{R'_{eq}} \right)^{-1}$$



$$R'''_{eq} = R_L + R''_{eq}$$

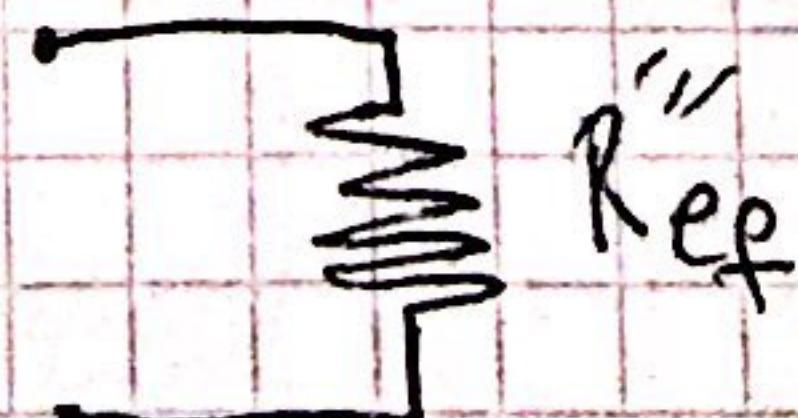

$$R_{EQ} = R_1 + \left(\frac{1}{R_1} + \frac{1}{R_1+R_0} \right)^{-1}$$

b)

$$R_0 = R_1 + \left(\frac{1}{R_1} + \frac{1}{R_1+R_0} \right)^{-1}$$

$$R_0 - R_1 = \left(\frac{1}{R_1} + \frac{1}{R_1+R_0} \right)^{-1}$$

$$\frac{1}{R_0 - R_1} = \frac{(R_1 + R_0) + R_1}{R_1(R_1 + R_0)}$$

$$\frac{R_1(R_1 + R_0)}{R_0 - R_1} = 2R_1 + R_0$$


$$R_1^2 + R_1 R_0 = 2R_1 R_0 + R_0^2 - 2R_1^2 - R_1 R_0$$

$$3R_1^2 - R_0^2 = 0$$

$$R_1 = \boxed{\frac{R_0}{\sqrt{3}}}$$

(4)

a)

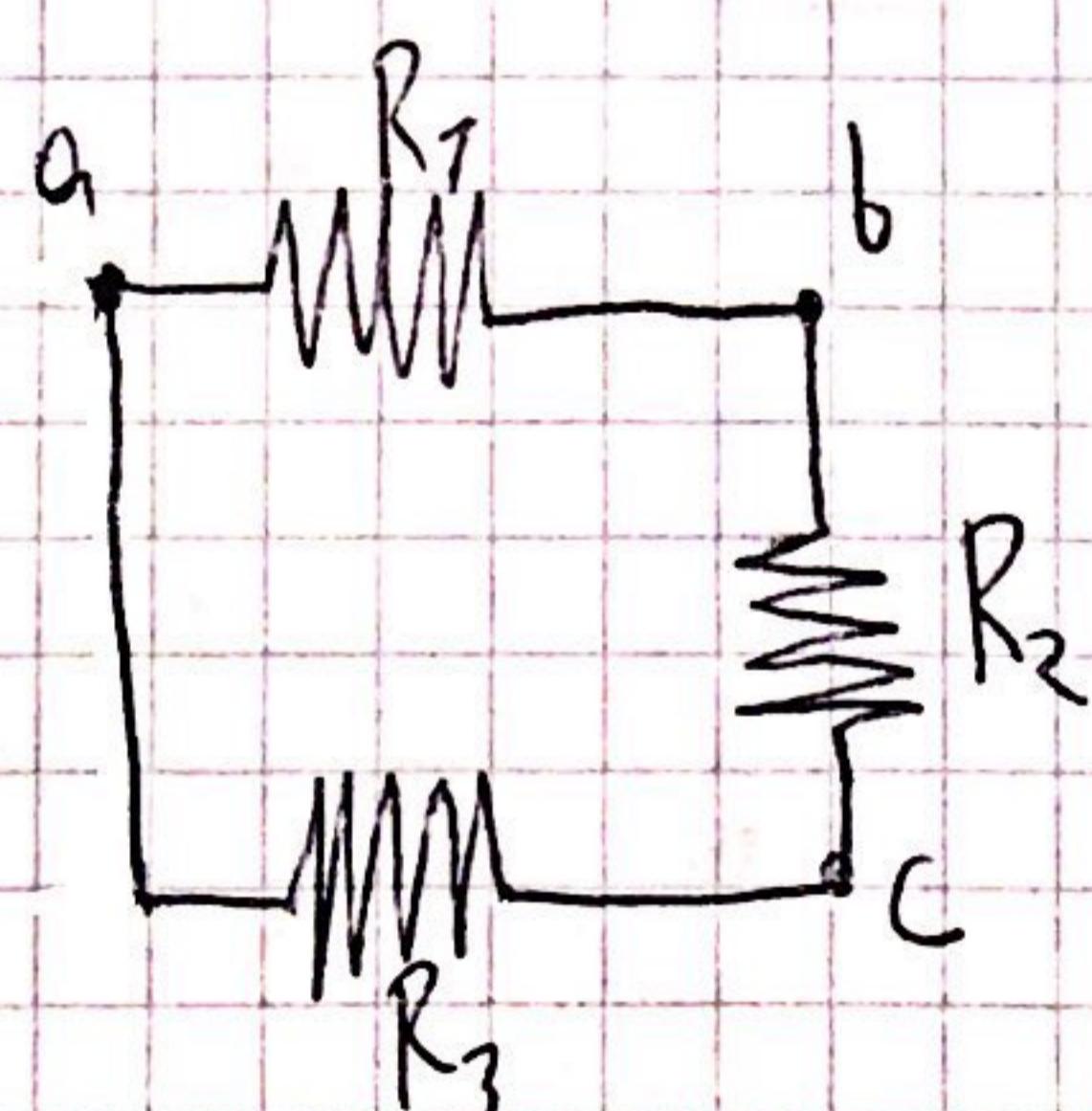


$$R_0 = R_1 = 34\Omega$$

$$R_0 = R_2 = 170\Omega$$

$$R_0 = R_3 = 85\Omega$$

R_{ab}

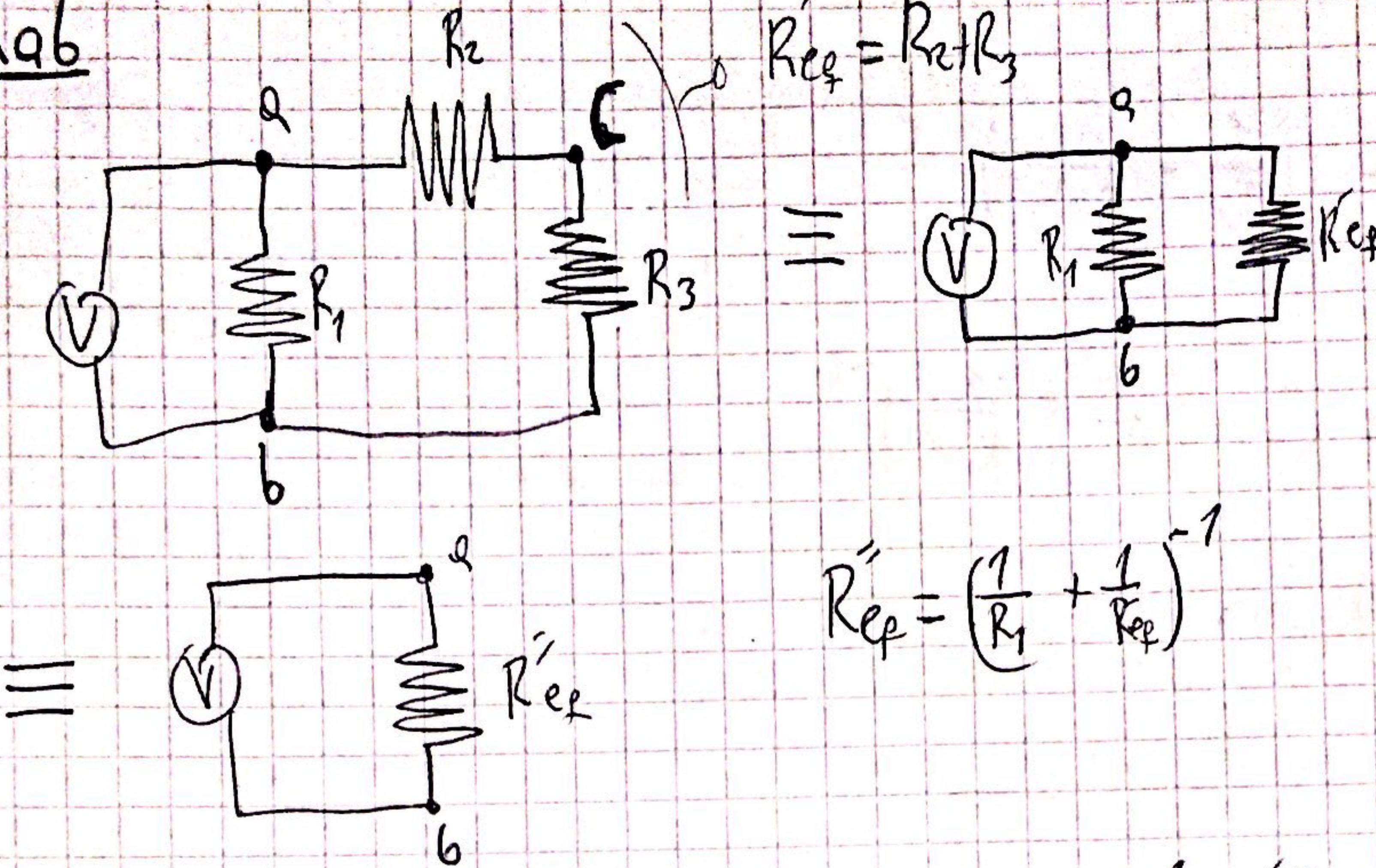


$$R'_{ref} = \left(\frac{1}{R_1} + \frac{1}{R'_{ref}} \right)^{-1}$$

$$R'_{ab} = R'_{ref} = \left(\frac{1}{R_1} + \frac{1}{R'_{ref}} \right)^{-1} = \left(\frac{1}{R_1} + \frac{1}{R_2 + R_3} \right)^{-1} = \left(\frac{R_2 + R_3 + R_1}{R_1(R_2 + R_3)} \right)^{-1}$$

$$= \left(\frac{289\Omega}{(255\Omega)345\Omega} \right)^{-1} = 30\Omega$$


R_{bc}

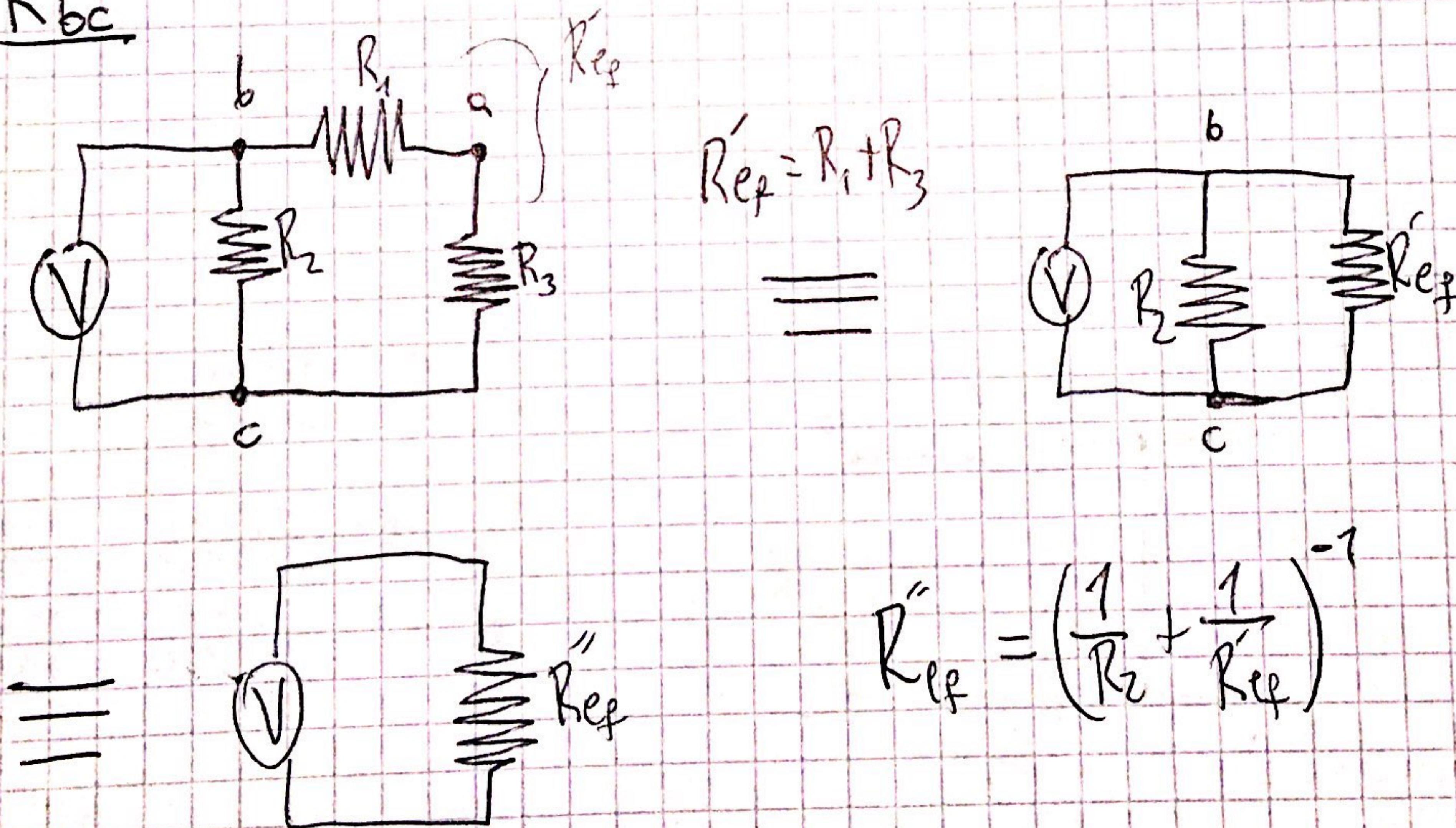

$$R'_{ref} = \left(\frac{1}{R_2} + \frac{1}{R'_{ref}} \right)^{-1}$$


$$R'_{bc} = R'_{ref} = \left(\frac{1}{R_2} + \frac{1}{R'_{ref}} \right)^{-1} = \left(\frac{1}{R_2} + \frac{1}{R_1 + R_3} \right)^{-1} = \left(\frac{R_1 + R_3 + R_2}{R_2(R_1 + R_3)} \right)^{-1} = \left(\frac{289\Omega}{(10\Omega)(11\Omega)} \right)^{-1}$$

$$= 70 \Omega$$

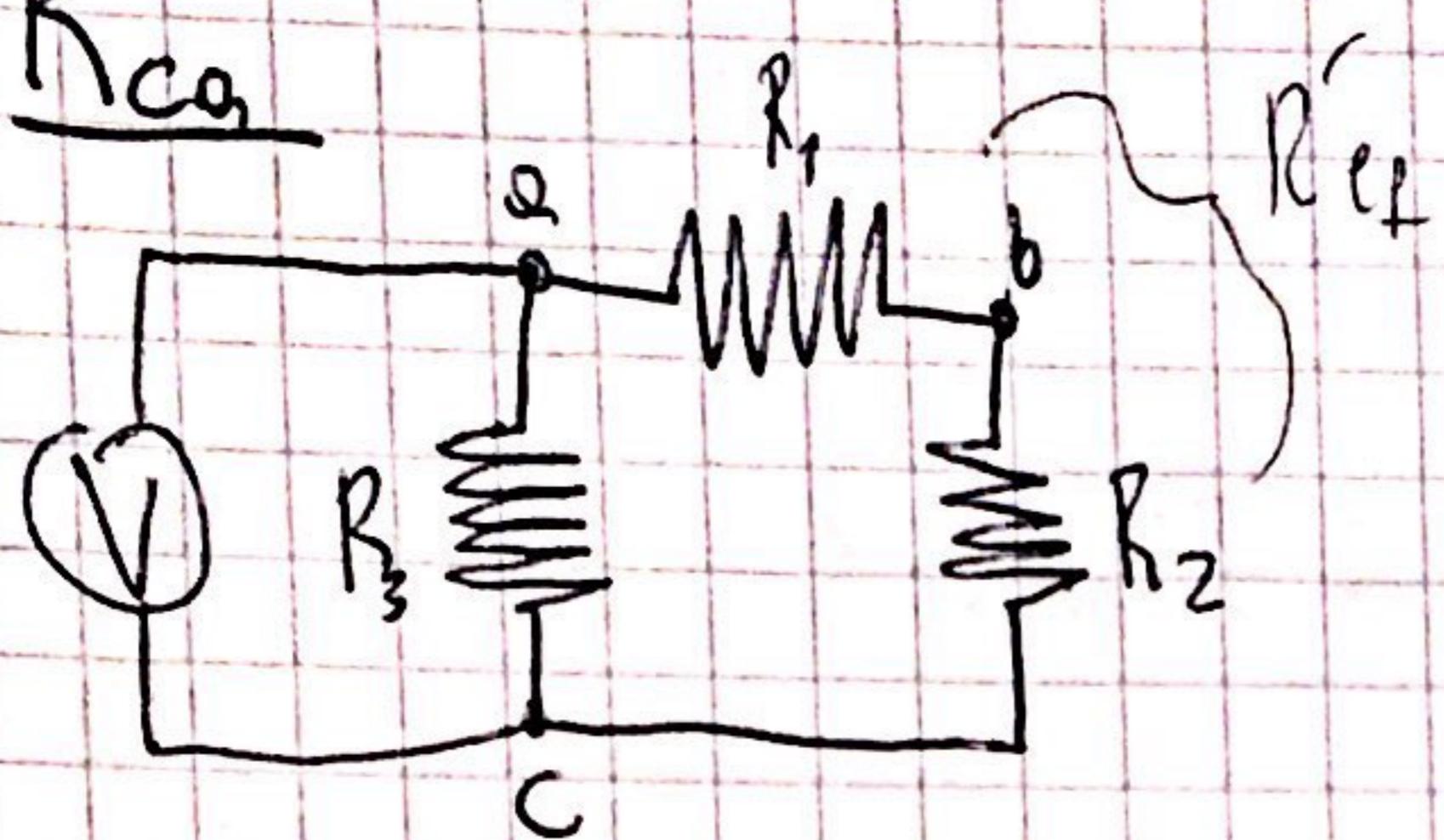 R_{ca} 


$$R'_ef = R_1 + R_2$$

=

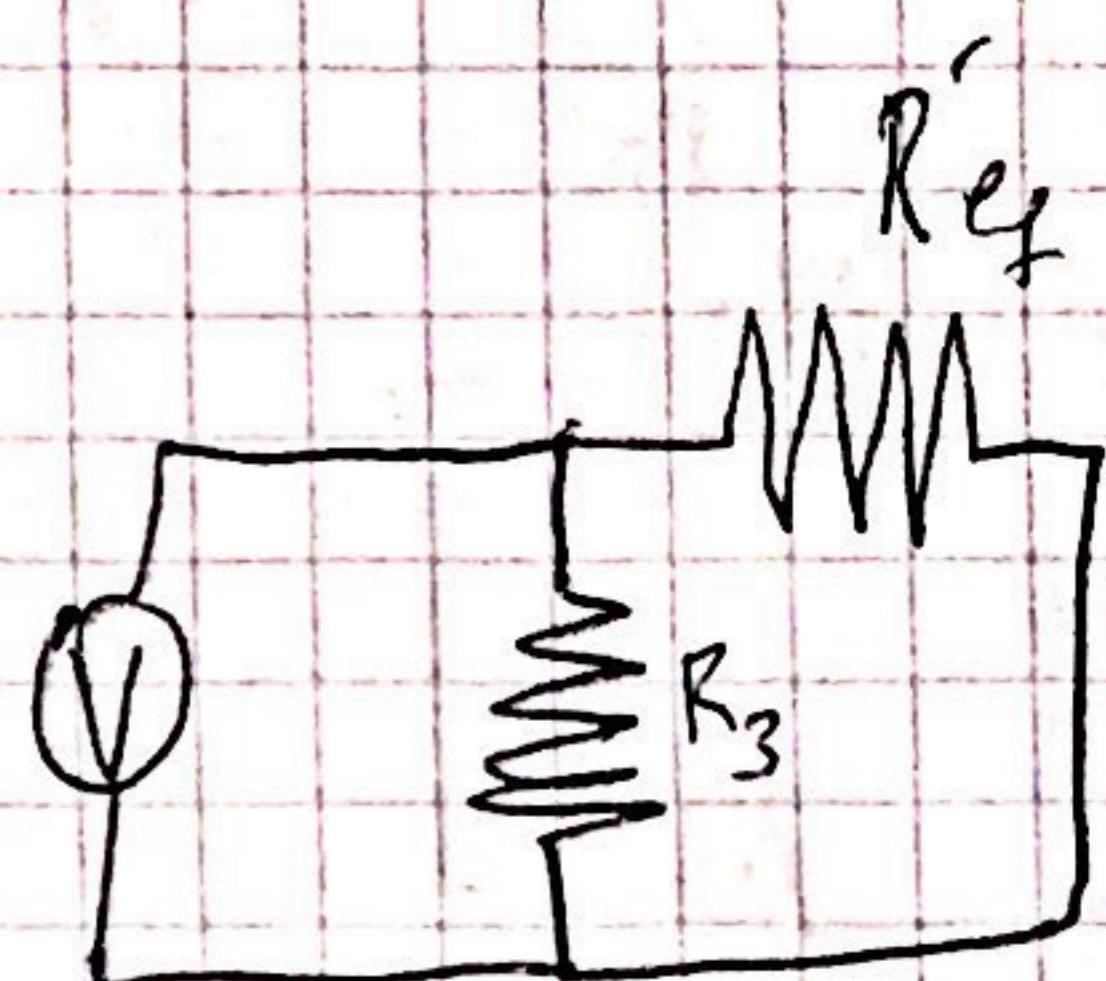


$$R'_ef = \left(\frac{1}{R_3} + \frac{1}{R'_ef} \right)^{-1}$$

=

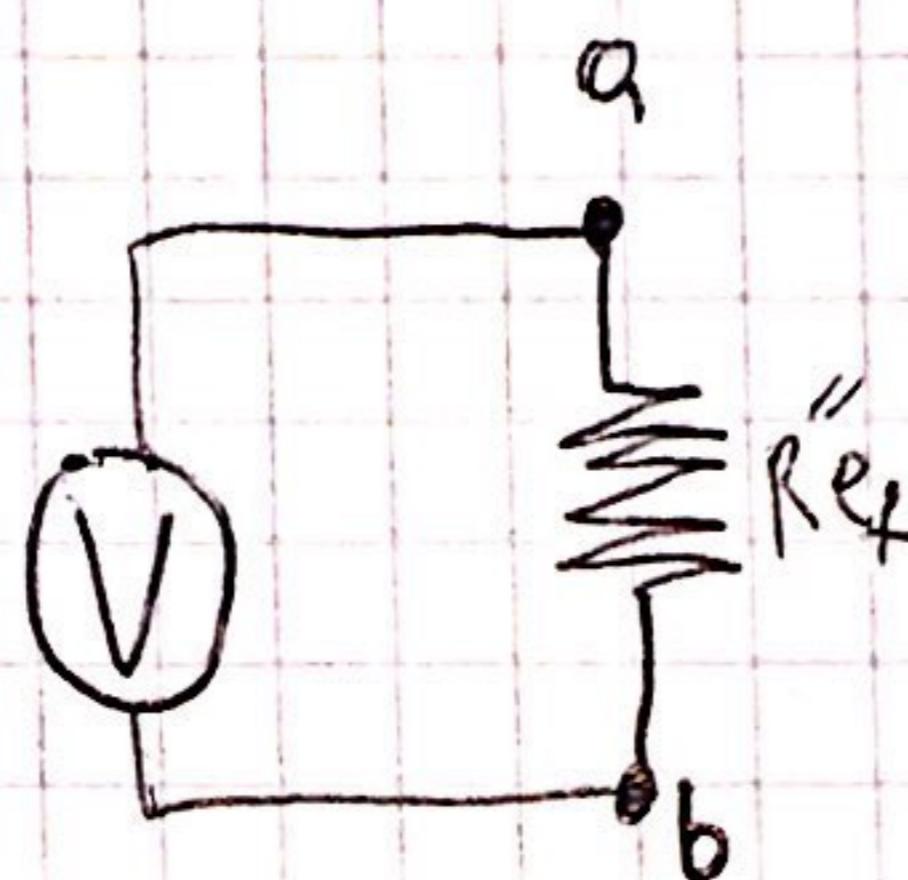

$$R_{ac} = R''ef = \left(\frac{1}{R_3} + \frac{1}{R'_ef} \right) = \left(\frac{R_1 + R_2 + R_3}{R_3(R_1 + R_2)} \right)^{-1} = \left(\frac{28\Omega}{85\Omega(20\Omega)} \right)^{-1} = 60\Omega$$


b)

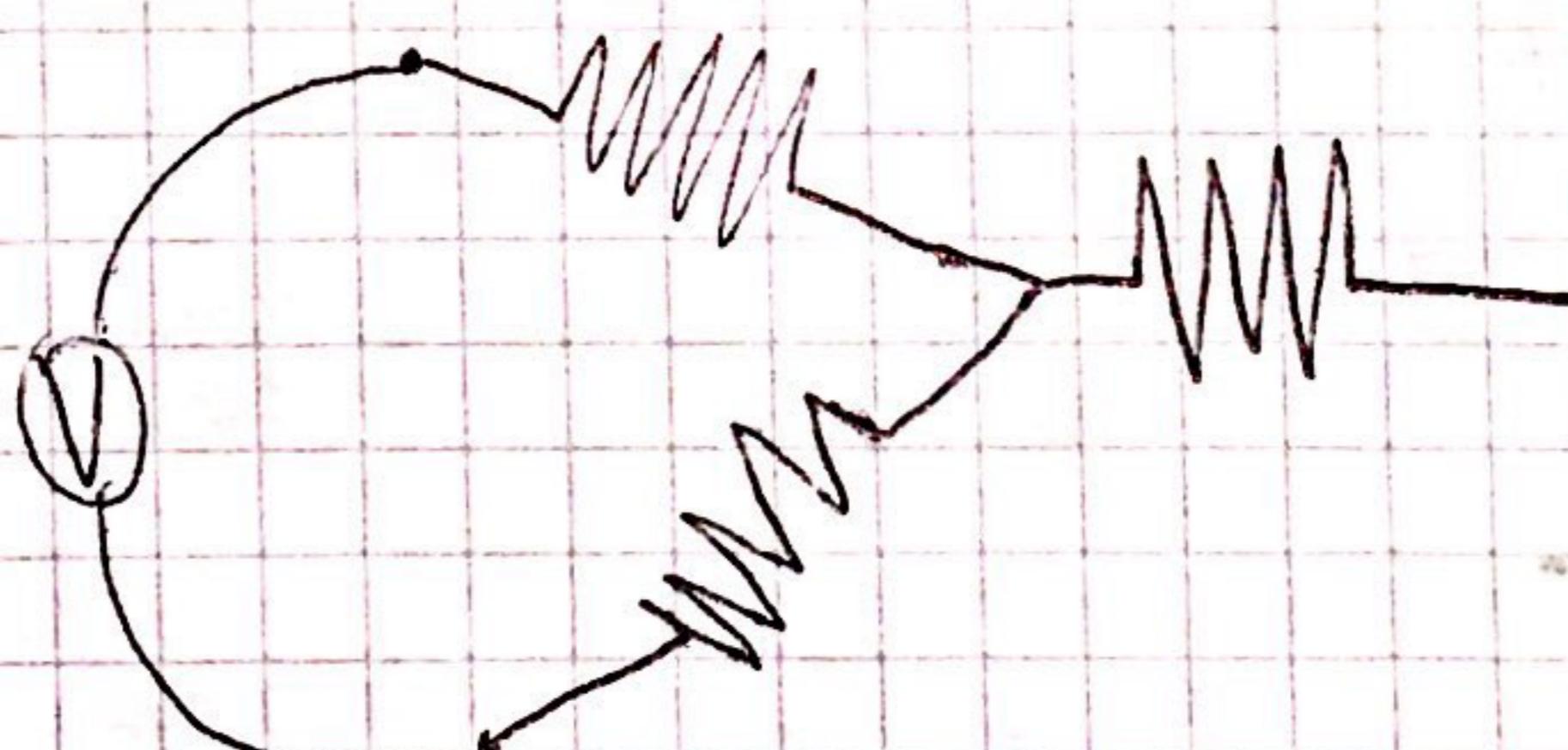


$$R_1 = 20\Omega$$

$$R_2 = 50\Omega$$

$$R_3 = 10\Omega$$

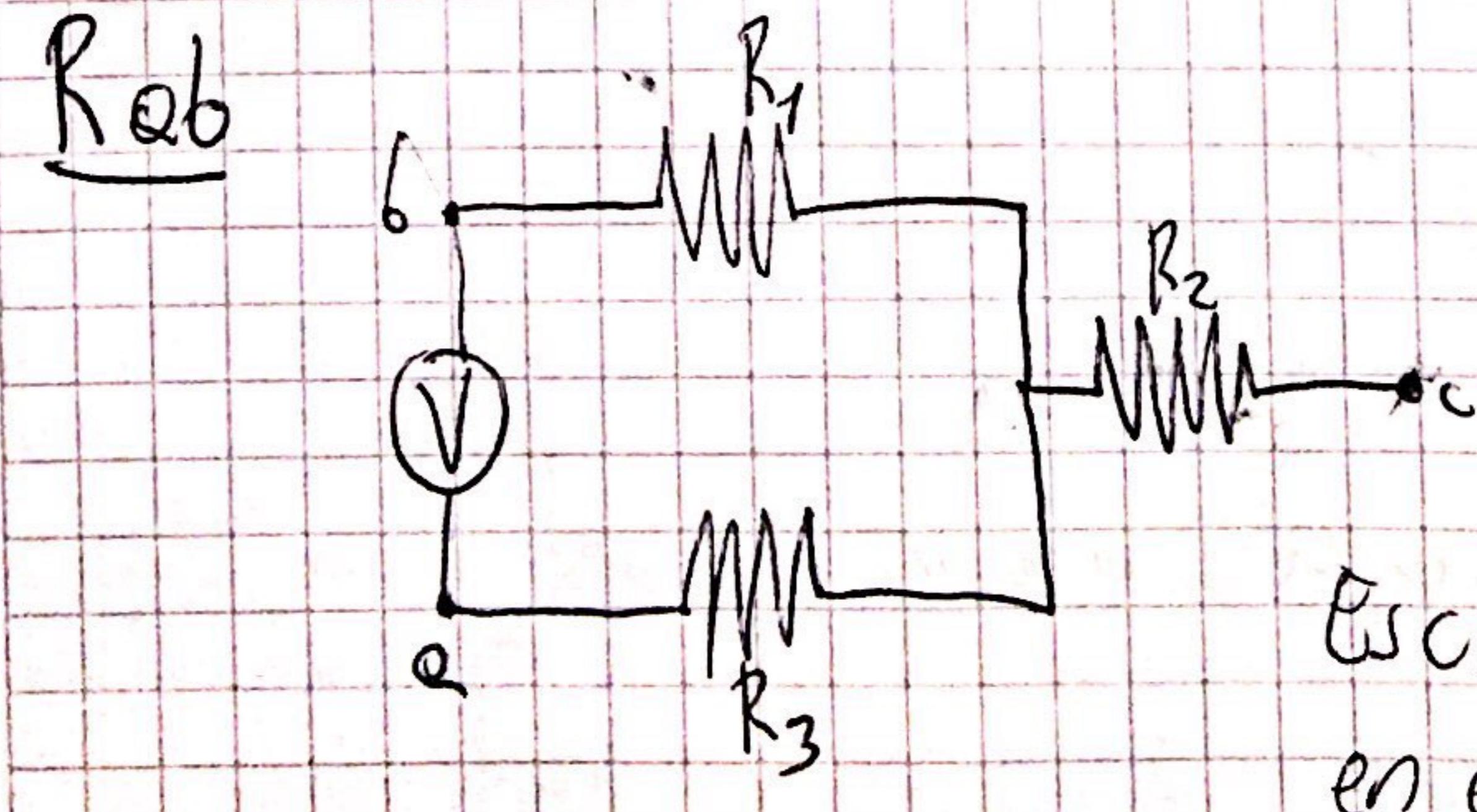
 R_{ab} 

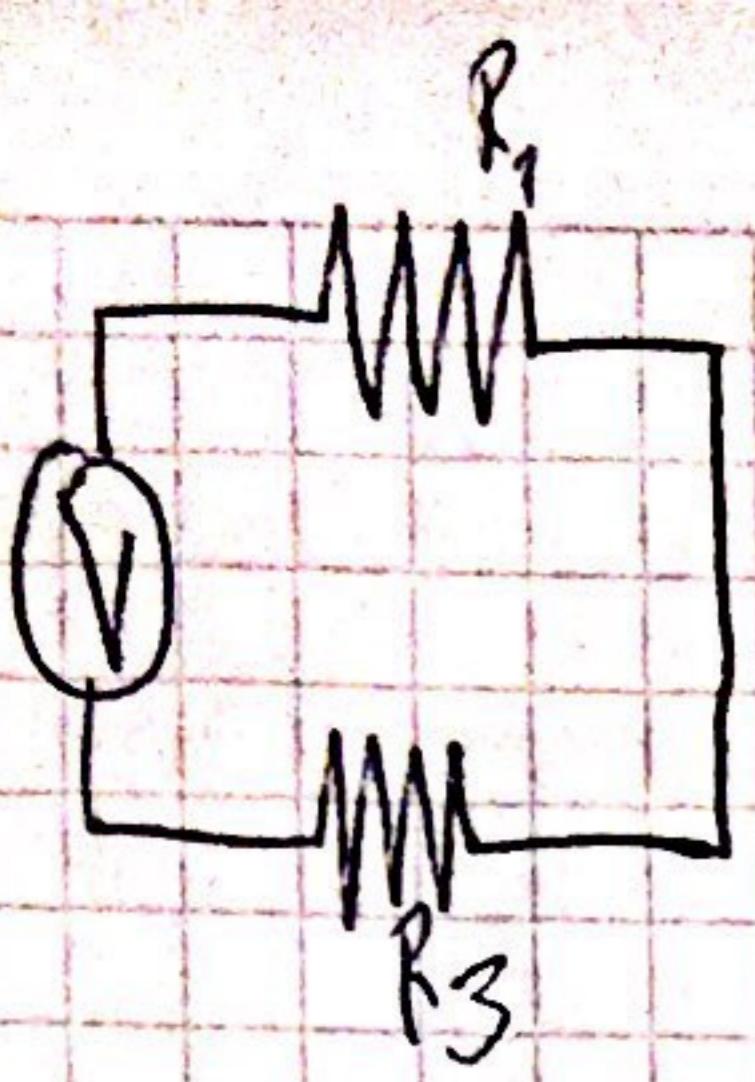Esclaro que R_2 no se involucra en el circuito.




$$R_{ab} \stackrel{?}{=} R_{eq} = R_1 + R_3 = 30\Omega \checkmark$$

R_{bc}

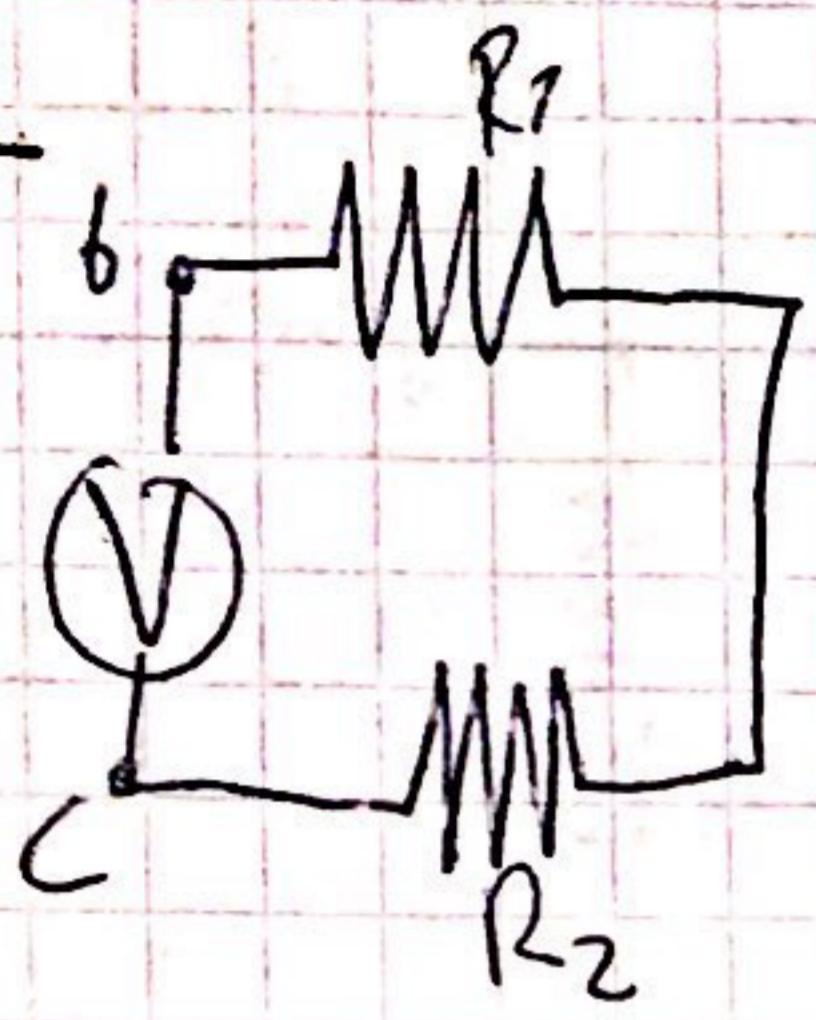

$$R_{bc} \stackrel{?}{=} R_{eq} = R_1 + R_2 = 70\Omega \checkmark$$

R_{ac}

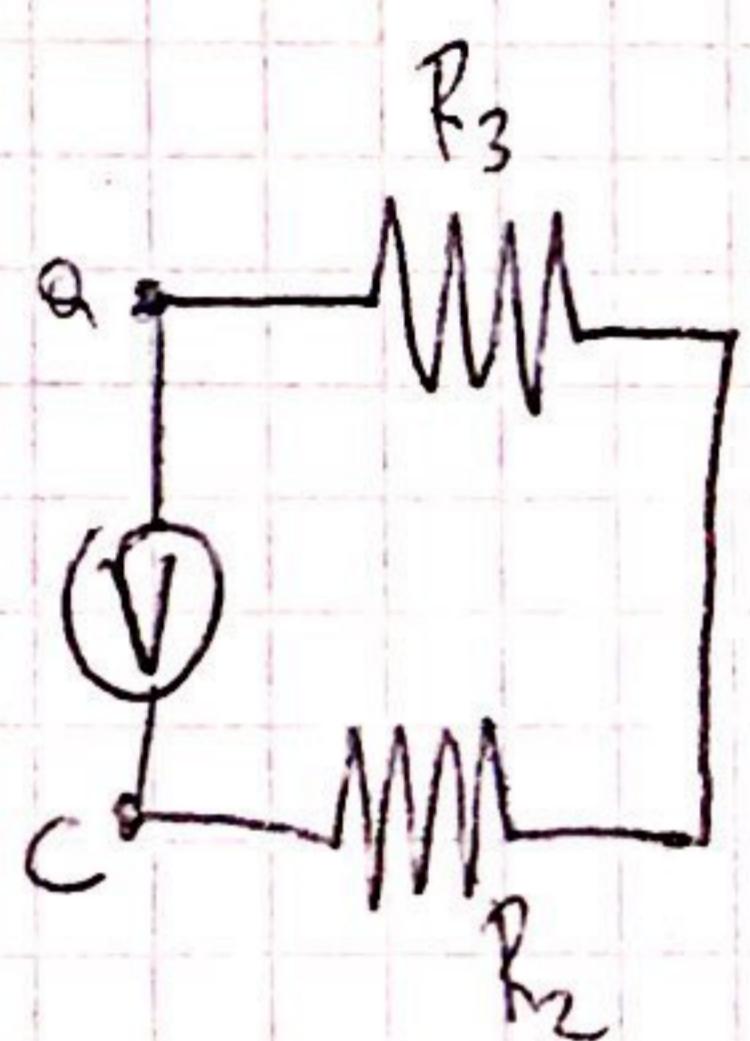


$$R_{ac} \stackrel{?}{=} R_{eq} = R_3 + R_2 = 60\Omega \checkmark$$

(5)

i) Se puede pensar como

dos capacitores en paralelo

$$C_{eq} = C_{1d} + C_{2d}$$

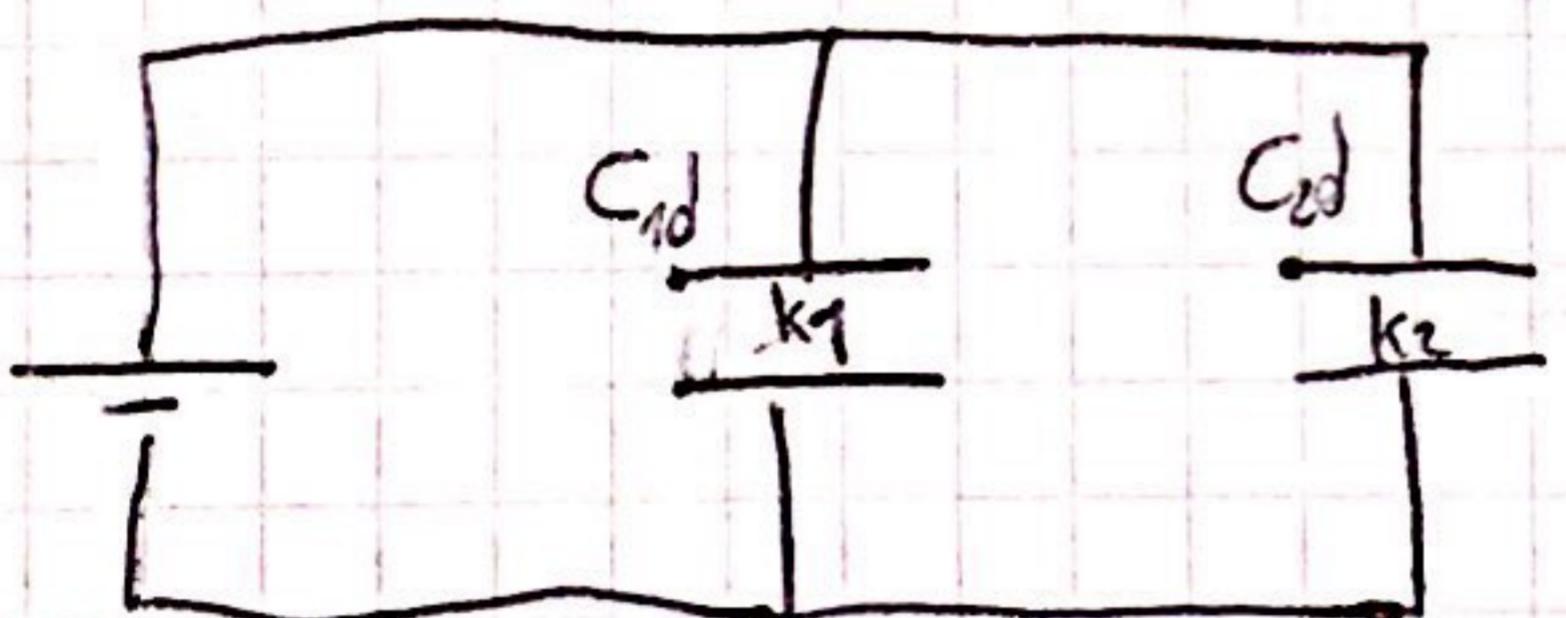


$$C_{1d} = \frac{A \cdot \epsilon_0}{2d} \cdot k_1 = \frac{A \epsilon_0}{2d} \cdot \frac{\epsilon_1}{\epsilon_0} = \frac{A \epsilon_1}{2d}$$

$$C_{2d} = \frac{A \epsilon_0}{2d} \cdot k_2 = \frac{A \epsilon_0}{2d} \cdot \frac{\epsilon_2}{\epsilon_0} = \frac{A \epsilon_2}{2d}$$

$$C_{eq} = C_{1d} + C_{2d} = \frac{A}{2d} (\epsilon_1 + \epsilon_2)$$

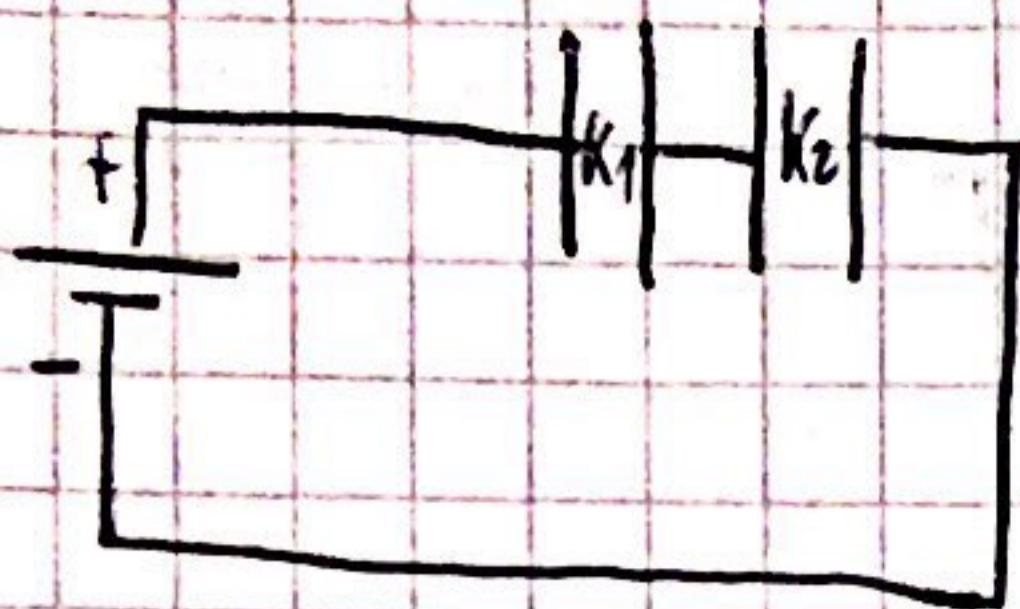ii) Se puede pensar como dos capacitores en serie.



$$C_1 = C_2 = \frac{\epsilon_0 A}{\frac{d}{2}} = \frac{2\epsilon_0 A}{d}$$


$$C_{1d} = \frac{2\epsilon_0 A}{d} \cdot k_1 = \frac{2\epsilon_0 A}{d}$$

$$C_{2d} = \frac{2\epsilon_0 A}{d} \cdot k_2 = \frac{2\epsilon_0 A}{d}$$

Entonces:

$$C_{ef} = \left(\frac{1}{C_{1d}} + \frac{1}{C_{2d}} \right)^{-1} = \frac{2d}{\epsilon_0} \left(\frac{1}{k_1} + \frac{1}{k_2} \right)^{-1}$$


6

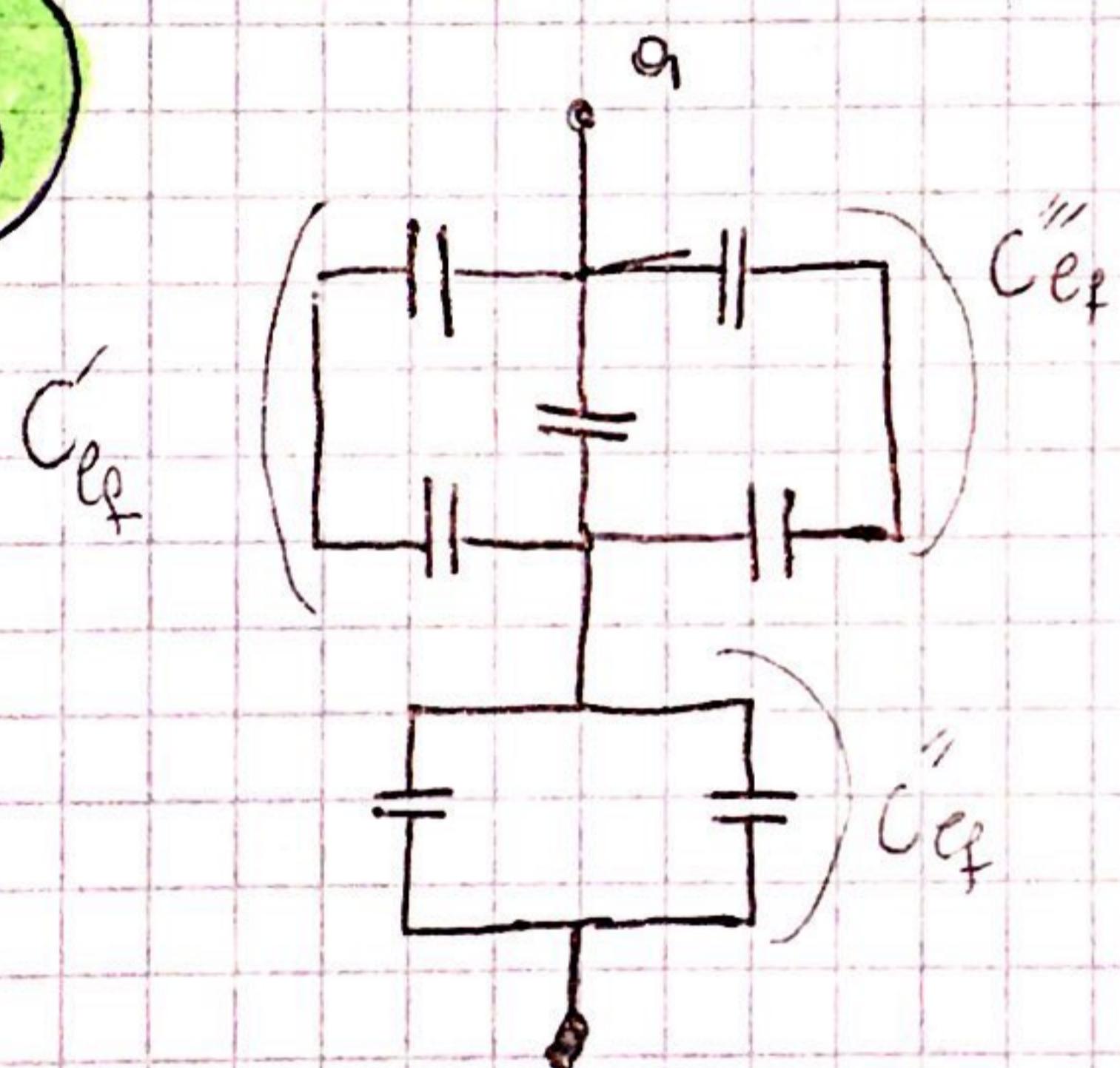


$$C'_{ef} = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)^{-1} = \frac{C_1 \cdot C_2}{C_1 + C_2}$$

$$C'_{ef} = C_2 + C_1 = 2C_2$$

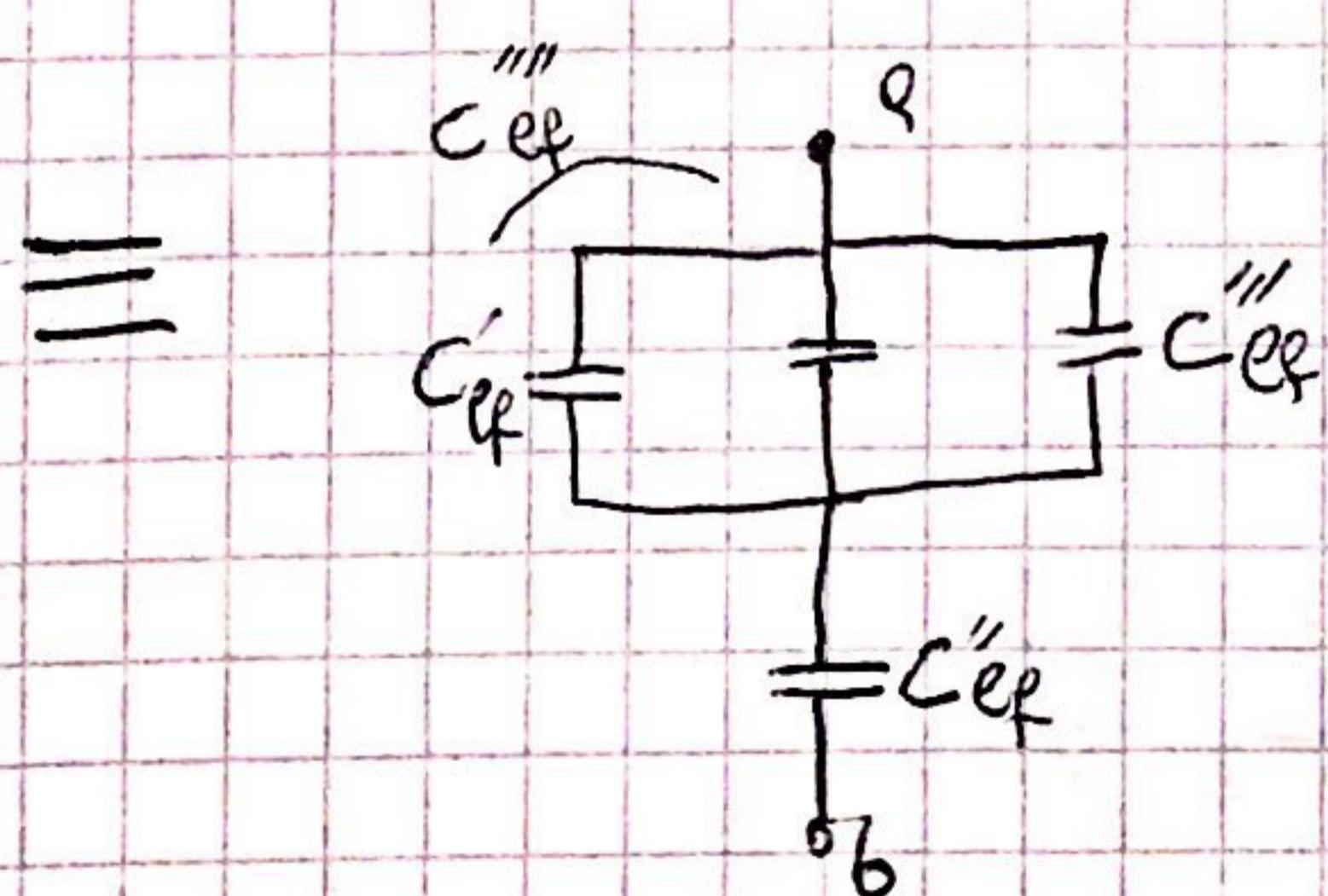
$$C'''_{ef} = C'_{ef} = \frac{C_1 \cdot C_2}{C_1 + C_2}$$



$$C'''_{ef} = C'_{ef} + C_3$$

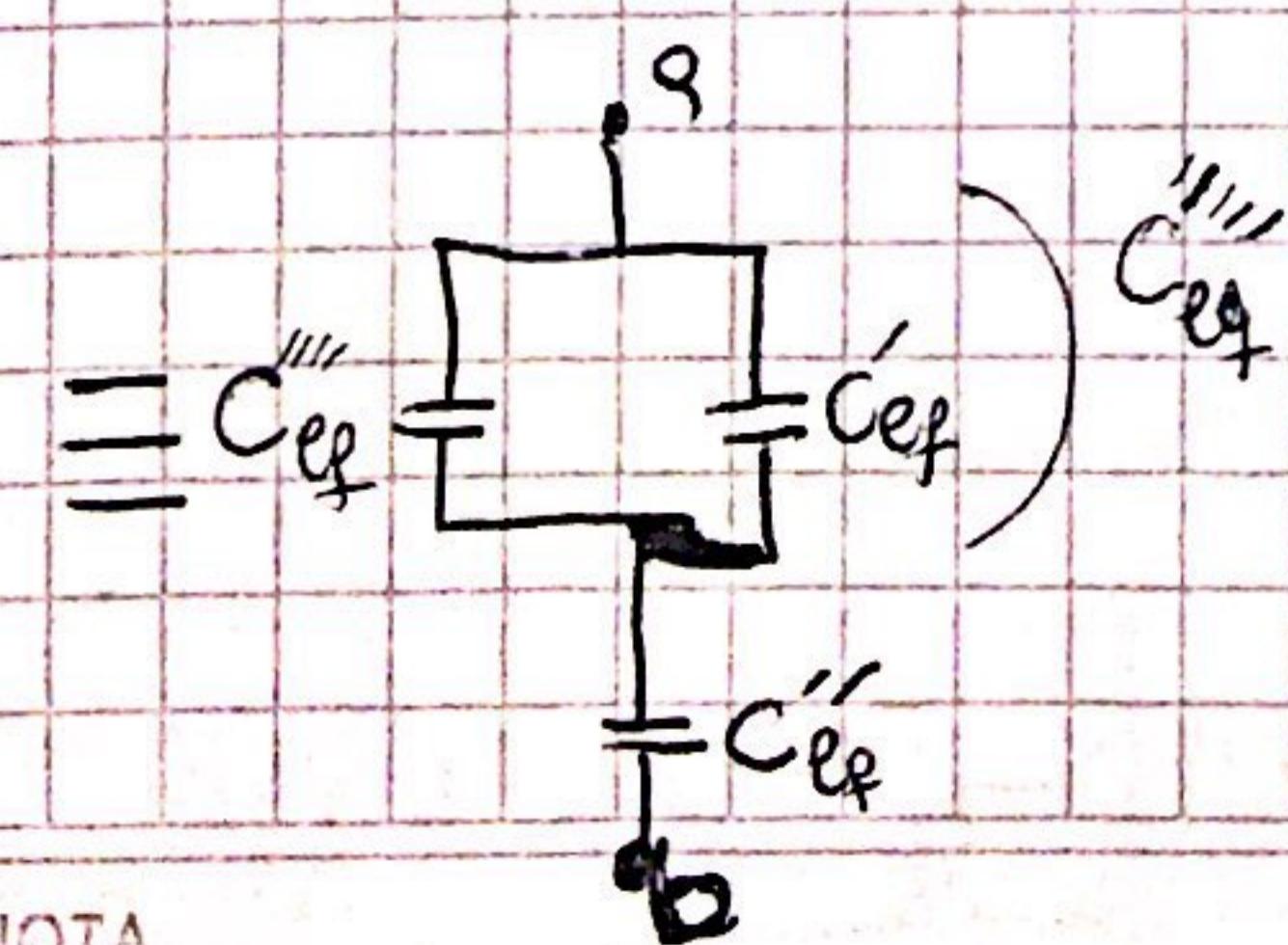

$$C'''_{ef} = C'_{ef} + C''_{ef}$$

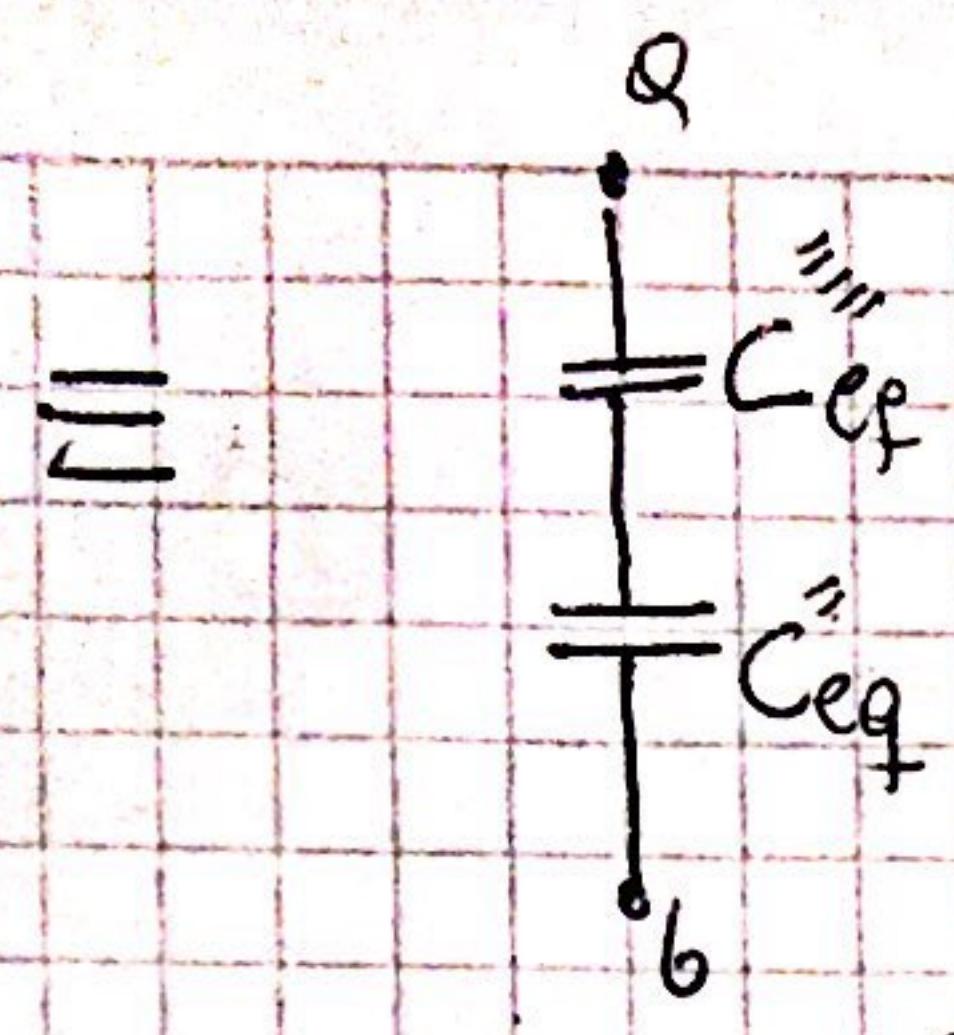

$$C_{EQ} = \left(\frac{1}{C_{eq}} + \frac{1}{C_{eq}} \right)^{-1} = \frac{C_{eq} \cdot C_{eq}}{C_{eq} + C_{eq}}$$

$$C'_{eq} = \frac{50}{7} \frac{\mu F^2}{\mu F} = \frac{10}{3} \mu F$$

$$C_{eq} = 20 \mu F$$

$$C''_{eq} = \frac{10}{3} \mu F$$


$$C'''_{eq} = \frac{10}{3} \mu F + 2 \mu F = \frac{16}{3} \mu F$$

$$C''''_{eq} = \frac{16}{3} \mu F + \frac{10}{3} \mu F = \frac{26}{3} \mu F$$

$$C_{EQ} = \frac{20 \mu F \cdot \frac{26}{3} \mu F}{\frac{26}{3} \mu F + 20 \mu F} = \frac{520 \mu F}{3} \cdot \frac{3}{86} \mu F = \frac{520}{86} \mu F \approx 6,04 \mu F$$

7

Serie

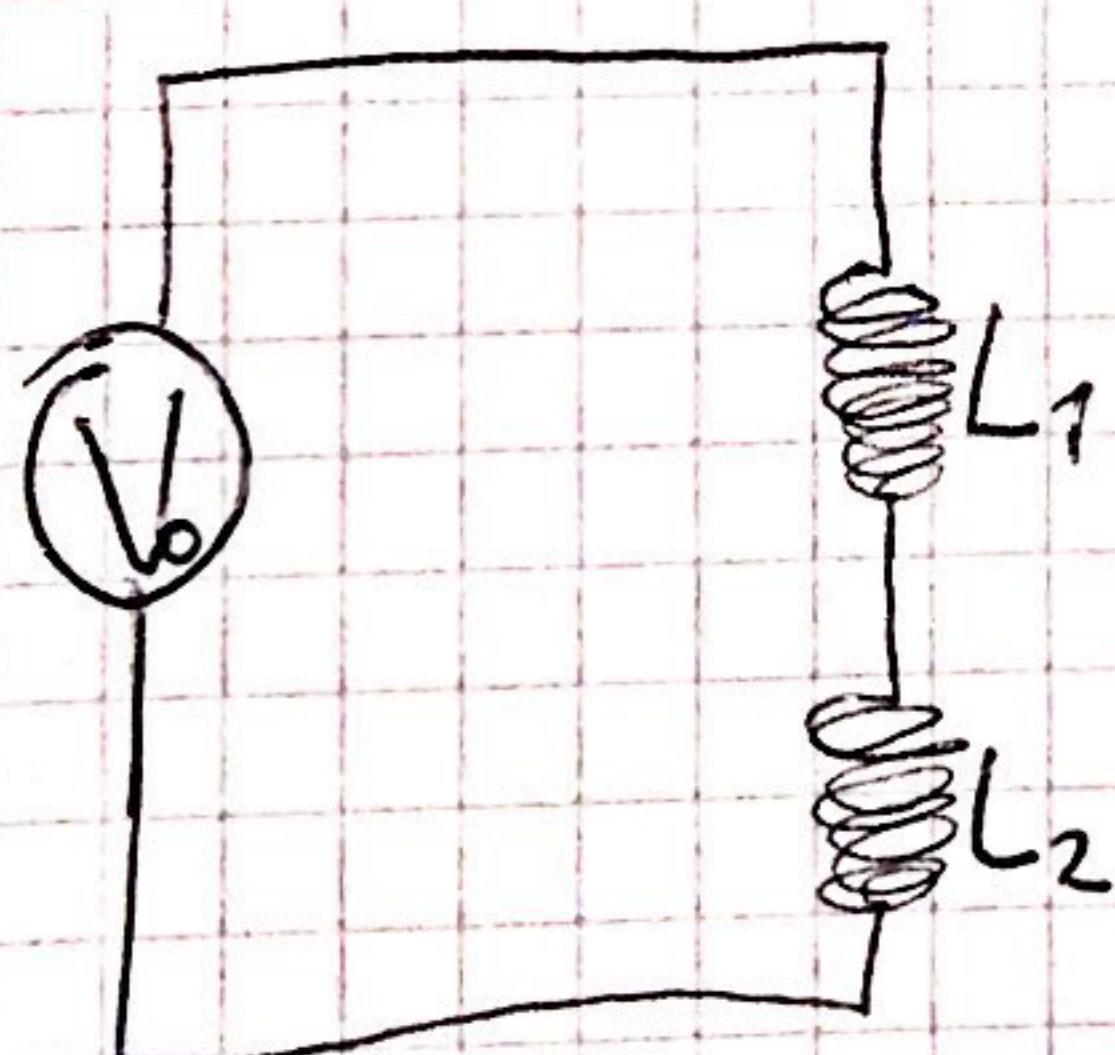

$$V_1 = -L_1 \frac{di}{dt}$$

$$V_2 = -L_2 \frac{di}{dt}$$

$$V = -L_{eq} \cdot \frac{di}{dt}$$


Dado que $V = V_1 + V_2$:

$$L \frac{di}{dt} = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} \implies L_{eq} = L_1 + L_2$$

HOJA N°

FECHA

Percaleb

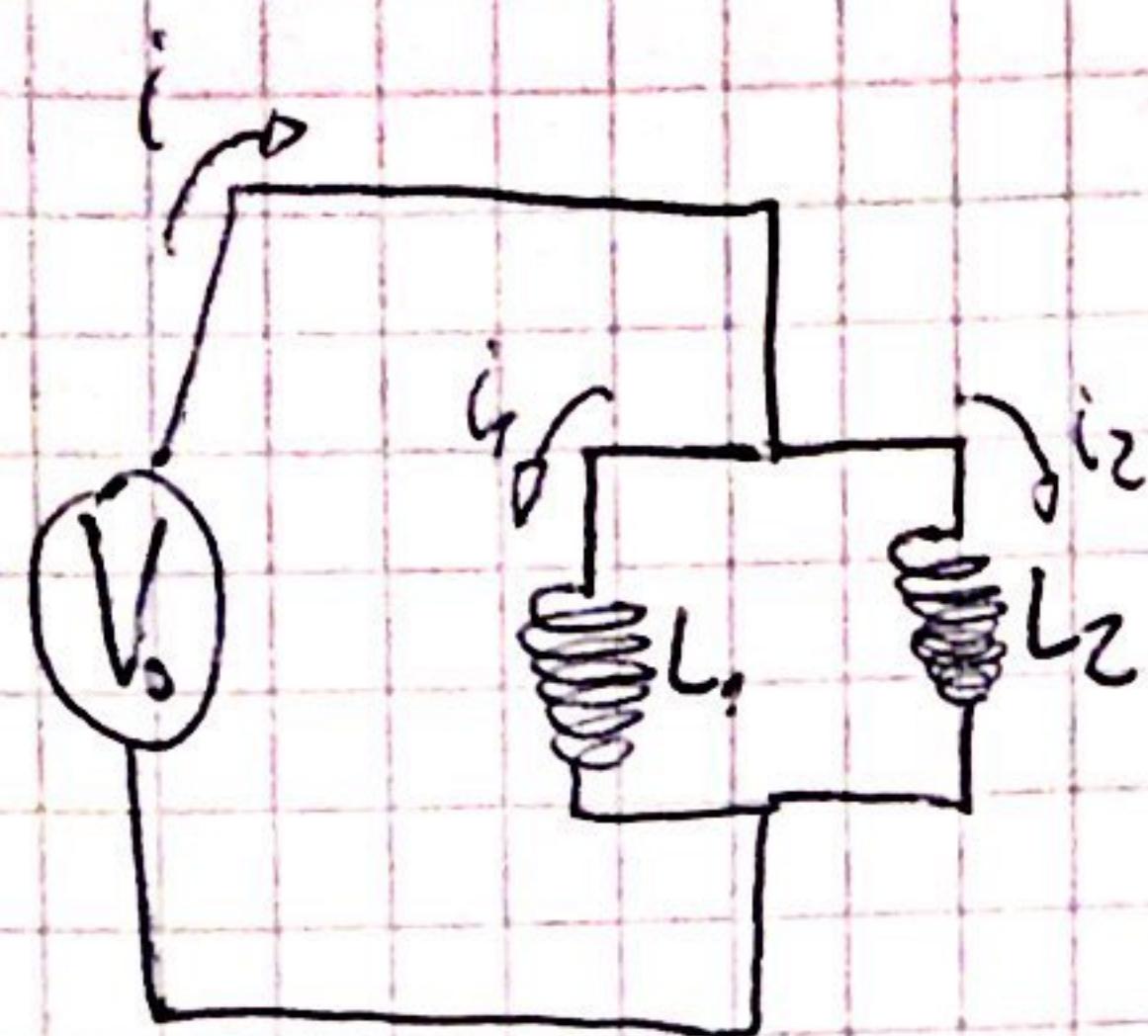

$$i = i_1 + i_2 \Rightarrow \frac{di}{dt} = \frac{di_1}{dt} + \frac{di_2}{dt}$$

$$V_0 = V_1 = V_2$$

Si las corrientes llegan a sus respectivas
máximas, no habrá más que una diferencia de voltaje

$$V_o = -L_{ef} \frac{di}{dt} = -L_{ef} \left(\frac{di_1}{dt} + \frac{di_2}{dt} \right)$$

$$= -L_{ef} \left(-\frac{V_1}{L_1} - \frac{V_2}{L_2} \right) = L \left(\frac{V_0}{L_1} + \frac{V_0}{L_2} \right)$$

$$\Rightarrow V_o = L_{eq}V_o \left(\frac{1}{L_1} + \frac{1}{L_2} \right)$$

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2}$$